

What is Impedance?

Worksheet

Impedance $Z = R + jX$ combines resistance R and reactance X ; its magnitude is $|Z| = \sqrt{R^2 + X^2}$, measured in ohms (Ω).

$$Z = \sqrt{R^2 + X^2}$$

Questions

1. Impedance combines resistance with:

- A) Reactance
- B) Current
- C) Power
- D) Voltage

2. The magnitude of impedance is given by:

- A) $R + X$
- B) $\sqrt{R^2 + X^2}$
- C) $R \times X$
- D) R / X

3. The formula for inductive reactance X_L is:

- A) $2\pi fL$
- B) $1/(2\pi fC)$
- C) $R + X$
- D) C

4. As frequency increases, capacitive reactance X_C :

- A) Increases
- B) Decreases
- C) Stays the same
- D) Becomes zero

5. A circuit has $R = 30 \Omega$ and capacitive reactance $X = 40 \Omega$. Find $|Z|$.

6. An inductor $L = 0.2 \text{ H}$ is driven at $f = 60 \text{ Hz}$. Find its reactance X_L .

7. A capacitor $C = 50 \text{ F}$ is driven at $f = 60 \text{ Hz}$. Find its reactance X_C .

8. Define: What is impedance?

9. Define: Unit of impedance?

10. Define: What is reactance?

Answer Key

1. A) Reactance - Impedance $Z = R + jX$ combines resistance R and reactance X .
2. B) $(R + X)$ - Since R and X are perpendicular in the phasor plane, the Pythagorean formula applies.
3. A) $2fL - XL = 2fL = L$, increasing with frequency.
4. B) Decreases - $XC = 1/(2fC)$, which decreases as f increases.
5. $|Z| = (R + X) = (30 + 40) = (900 + 1600) = 2500 = 50$
6. $XL = 2fL = 2 \cdot 60 \cdot 0.2 = 75.4$
7. $XC = 1/(2fC) = 1/(2 \cdot 60 \cdot 0.00005) = 1/0.01885 = 53.05$
8. The total opposition an AC circuit offers to current: $Z = R + jX$, combining resistance and reactance.
9. Ohms (Ω), same as resistance.
10. The opposition to current from inductors and capacitors, which depends on frequency.

Bounlu

All cards, step-by-step solutions and an AI tutor are in the Notek app.
Promy turns exam dates into automatic reminders.