

# What are Logic Gates?

## Worksheet

A logic gate is a digital circuit that performs a single Boolean logic operation (AND, OR, NOT, XOR, etc.) on one or more binary inputs to produce one binary output, defined by its truth table.

## Questions

1. What is the output of an AND gate when  $A=1$  and  $B=0$ ?

- A) 1
- B) 0
- C) Undefined
- D) Depends on clock

2. Which gate outputs 1 whenever at least one input is 1?

- A) AND
- B) NOT
- C) OR
- D) XNOR

3. What does a NOT gate do to a single input of 0?

- A) Outputs 0
- B) Outputs 1
- C) Outputs undefined
- D) Outputs 2

4. Which gate is called 'universal' because any Boolean function can be built from it alone?

- A) OR
- B) XOR
- C) NAND
- D) Buffer

5. An AND gate has inputs  $A=1$  and  $B=1$ . What is the output  $Y$ ?

6. An OR gate has inputs  $A=0$  and  $B=1$ . What is the output  $Y$ ?

7. A NOT gate (inverter) receives input  $A=1$ . What is the output  $Y$ ?

8. Define: What does an AND gate output?

9. Define: What does an OR gate output?

10. Define: What does a NOT gate do?

## Answer Key

1. B) 0 - AND requires ALL inputs to be 1; since B=0, output is 0.
2. C) OR - OR outputs 1 if any input is 1.
3. B) Outputs 1 - NOT inverts the input, so 0 becomes 1.
4. C) NAND - NAND (and NOR) are functionally complete - any logic circuit can be built using only NAND gates.
5. AND rule:  $Y = A B$  (1 only if both inputs are 1) A=1, B=1  $Y = 11 = 1$  Output  $Y = 1$
6. OR rule:  $Y = A + B$ , output 1 if at least one input is 1 A=0, B=1 at least one input is 1 Output  $Y = 1$
7. NOT rule:  $Y = (\text{flips the input})$  A = 1 flip to 0 Output  $Y = 0$
8. 1 only when ALL inputs are 1; otherwise 0.
9. 1 when AT LEAST ONE input is 1; 0 only if all inputs are 0.
10. Inverts the input: 0 becomes 1, 1 becomes 0 (also called an inverter).

### **Bounlu**

All cards, step-by-step solutions and an AI tutor are in the Notek app.  
Promy turns exam dates into automatic reminders.