

What is an Operational Amplifier?

Worksheet

An op-amp amplifies the difference between its inputs; with feedback its gain is set by external resistors, e.g. $V_{out} = (R_f/R_{in})V_{in}$ for the inverting configuration.

$$V_{out} = A(V_{+} - V_{-})$$

Questions

1. An ideal op-amp has input impedance:

- A) Zero
- B) Infinite
- C) 1 k
- D) Negative

2. The inverting amplifier gain formula is:

- A) R_f/R_{in}
- B) R_f/R_{in}
- C) $1 + R_f/R_{in}$
- D) R_{in}/R_f

3. The non-inverting amplifier gain formula is:

- A) R_f/R_{in}
- B) R_f/R_{in}
- C) $1 + R_f/R_{in}$
- D) $1 R_f/R_{in}$

4. In an inverting amplifier, the output is:

- A) In phase with the input
- B) 180 out of phase with the input
- C) 90 shifted
- D) There is no output

5. An inverting amplifier has $R_f = 10 \text{ k}$, $R_{in} = 1 \text{ k}$ and $V_{in} = 0.5 \text{ V}$. Find V_{out} .

6. A non-inverting amplifier has $R_f = 20 \text{ k}$, $R_{in} = 5 \text{ k}$ and $V_{in} = 1 \text{ V}$. Find V_{out} .

7. An op-amp has open-loop gain $A = 100,000$ and inputs $V_{+} = 2.0001 \text{ V}$, $V_{-} = 2 \text{ V}$. Find V_{out} .

8. Define: What is an op-amp?

9. Define: What are the ideal op-amp assumptions?

10. Define: Formula for inverting amplifier gain?

Answer Key

1. B) Infinite - Ideal op-amps draw essentially no input current, implying infinite input impedance.
2. B) R_f/R_{in} - The inverting configuration gain is $A_v = R_f/R_{in}$, with a sign inversion.
3. C) $1 + R_f/R_{in}$ - Non-inverting gain is always at least 1: $A_v = 1 + R_f/R_{in}$.
4. B) 180 out of phase with the input - The inverting configuration flips the sign, producing a 180 phase shift.
5. $V_{out} = (R_f/R_{in})V_{in} = (10/1)0.5 = 5 \text{ V}$
6. $\text{Gain} = 1 + R_f/R_{in} = 1 + 20/5 = 5$ $V_{out} = 5 \cdot 1 = 5 \text{ V}$
7. $V_{out} = A(V_+ - V_-) = 100000 \cdot 0.0001 = 10 \text{ V}$ (would saturate near the supply rail in practice)
8. A high-gain differential voltage amplifier IC with two inputs and one output.
9. Infinite open-loop gain, infinite input impedance, and zero output impedance.
10. $A_v = R_f/R_{in}$.

Bounlu

All cards, step-by-step solutions and an AI tutor are in the Notek app.
Promy turns exam dates into automatic reminders.