

What is a Transistor?

Worksheet

A transistor is a three-terminal semiconductor device that amplifies current or acts as an electronic switch; in a BJT, collector current $I_C = \beta I_B$.

$$I_C = \beta I_B$$

Questions

1. How many terminals does a standard BJT transistor have?

- A) 2
- B) 3
- C) 4
- D) 1

2. β in a transistor represents:

- A) Voltage gain
- B) Current gain
- C) Power gain
- D) Resistance

3. The formula for collector current in terms of I_B is:

- A) $I_C = I_B / \beta$
- B) $I_C = I_B$
- C) $I_C = \beta I_B$
- D) $I_C = I_B \beta$

4. In an NPN transistor, the majority charge carriers are:

- A) Electrons
- B) Holes
- C) Protons
- D) Ions

5. A BJT has $\beta = 150$ and $I_B = 0.02$ mA. Find the collector current I_C .

6. A transistor has $I_C = 100$ mA and $\beta = 100$. Find the base current I_B .

7. A BJT switch has $V_{in} = 5$ V, $V_{be} = 0.7$ V and base resistor $R_b = 10$ k. Find I_B .

8. Define: What is a transistor?

9. Define: What are the three terminals of a BJT?

10. Define: What does β represent?

Answer Key

1. B) 3 - A BJT has three terminals: base, collector and emitter.
2. B) Current gain - is the current gain, the ratio I_c/I_b .
3. B) $I_c = I_b$ - Collector current equals the current gain times the base current.
4. A) Electrons - NPN transistors conduct mainly via electrons in the n-type regions.
5. $I_c = I_b = 150 \cdot 0.02 = 3 \text{ mA}$
6. $I_b = I_c / \beta = 100 / 100 = 1 \text{ mA}$
7. $I_b = (V_{in} - V_{be}) / R_b = (5 - 0.7) / 10000 = 4.3 / 10000 = 0.00043 \text{ A} = 0.43 \text{ mA}$
8. A semiconductor device that amplifies or switches electronic signals.
9. Base, Collector, and Emitter.
10. The current gain - the ratio of collector current to base current, I_c/I_b .

Bounlu

All cards, step-by-step solutions and an AI tutor are in the Notek app.
Promy turns exam dates into automatic reminders.