

# What is Electric Power?

## Worksheet

Electric power is the rate of electrical energy transfer:  $P = VI$ , measured in watts (W). It can also be written as  $P = IR$  or  $P = V/R$  using Ohm's law.

$$P = VI$$

## Questions

1. A device uses 220 V and draws 3 A. What is its power?

- A) 660 W
- B) 73.3 W
- C) 223 W
- D) 217 W

2. Which formula for power uses resistance directly with current?

- A)  $P = V/I$
- B)  $P = IR$
- C)  $P = V+I$
- D)  $P = I/R$

3. What is the SI unit of electric power?

- A) Joule
- B) Volt
- C) Watt
- D) Ampere

4. A 60 W bulb operates at 12 V. What current does it draw?

- A) 0.2 A
- B) 5 A
- C) 720 A
- D) 48 A

5. A lamp is connected to a 220 V mains supply and draws a current of 0.5 A. Find its power.

6. An electric heater rated at 1000 W is plugged into a 220 V outlet. Find the current it draws.

7. A motor coil has resistance 5 and carries a current of 2 A. Find the power dissipated.

8. Define: What is the formula for electric power?

9. Define: What is the unit of electric power?

10. Define: How do you find power using resistance?

## Answer Key

1. A)  $660 \text{ W} - P = VI = 220 \times 3 = 660 \text{ W}$ .
2. B)  $P = IR$  - From Ohm's law,  $P = IR$ .
3. C) Watt - Power is measured in watts (joules per second).
4. B)  $5 \text{ A} - I = P/V = 60/12 = 5 \text{ A}$ .
5.  $P = VI$  |  $P = 220 \times 0.5$  |  $P = 110 \text{ W}$
6.  $P = VI$  |  $I = P/V$  |  $I = 1000/220$  |  $4.55 \text{ A}$
7.  $P = IR$  |  $P = 2 \times 5$  |  $P = 10 \text{ W}$
8.  $P = VI$ , where P is in watts, V in volts, I in amps.
9. The watt (W), equal to one joule per second.
10.  $P = IR$  or  $P = V/R$ , derived from Ohm's law  $V = IR$ .

### Bounlu

All cards, step-by-step solutions and an AI tutor are in the Notek app.  
Promy turns exam dates into automatic reminders.